

07 - Latches and Flip-flops

1. Characteristic equations and completed tables for D, JK, T flip-flops

Characteristic equations:

$$q_{n+1}^D = d$$

$$q_{n+1}^{JK} = j \cdot \overline{q_n} + \overline{k} \cdot q_n$$

$$q_{n+1}^T = t \cdot \overline{q_n} + \overline{t} \cdot q_n$$

clk	d	q(n)	q(n+1)	Comments
↑	0	0	0	Remember/hold values, no change
↑	0	1	0	Input signal is sampled at the rising edge of clk and stored to FF
↑	1	0	1	Input signal is sampled at the rising edge of clk and stored to FF
↑	1	1	1	Remember/hold values, no change

clk	j	k	q(n)	q(n+1)	Comments
↑	0	0	0	0	No change
↑	0	0	1	1	No change
↑	0	1	0	0	Reset
↑	0	1	1	0	Reset
↑	1	0	0	1	Set
↑	1	0	1	1	Set
↑	1	1	0	1	Toggle
↑	1	1	1	0	Toggle

clk	t	q(n)	q(n+1)	Comments
↑	0	0	0	No change
↑	0	1	1	No change
↑	1	0	1	Invert (Toggle)
↑	1	1	0	Invert (Toggle)

2. D latch

VHDL code listing of the process p_d_latch:

```
p_d_latch : process (d, arst, en)
begin
    if (arst = '1') then
        q <= '0';
        q_bar <= '1';
    elsif (en = '1') then
        q <= d;
        q_bar <= not d;
    end if;
end process p_d_latch;
```

Listing of VHDL reset and stimulus processes from the testbench tb_d_latch.vhd file:

```
p_stimulus : process
begin
    report "Stimulus process started" severity note;

    s_en <= '0';
    s_d <= '0';

    --d sequence
    wait for 10ns;
    s_d <= '1';
    wait for 10ns;
    s_d <= '0';
    wait for 10ns;
    s_d <= '1';
    wait for 10ns;
    s_d <= '0';
    wait for 10ns;
    s_d <= '1';
    wait for 10ns;
    s_d <= '0';
    wait for 10ns;
    s_d <= '1';
    wait for 10ns;
    s_d <= '0';

    s_en <= '1';

    wait for 3ns;
    assert(s_q = '0' and s_q_bar = '1')
    report "chyba" severity error;

    --d sequence
    wait for 7ns;
```


```
s_d <= '1';
wait for 10ns;
s_d <= '0';
wait for 10ns;
s_d <= '1';
wait for 10ns;
s_d <= '0';
wait for 10ns;
s_d <= '1';
wait for 10ns;
s_d <= '0';
wait for 10ns;
s_d <= '1';
wait for 5ns;
s_en <= '0';
wait for 5ns;
s_d <= '0';
assert(s_q = '1' and s_q_bar = '0')
report "chyba latch" severity error;

--d sequence
wait for 10ns;
s_d <= '1';
wait for 10ns;
s_d <= '0';
wait for 10ns;
s_d <= '1';
wait for 10ns;
s_d <= '0';
wait for 10ns;
s_d <= '1';
wait for 10ns;
s_d <= '0';

s_en <= '1';

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;
```

 Screenshot with simulated time waveforms:



3. Flip-flops

VHDL code listing of the processes for D type flip-flop with an async reset:

```
p_d_ff_arst : process (clk, arst)
begin
    if (arst = '1') then
        q      <= '0';
        q_bar <= '1';
    elsif rising_edge(clk) then
        q      <= d;
        q_bar <= not d;
    end if;
end process p_d_ff_arst;
```

VHDL code listing of the processes for D type flip-flop with a sync reset:

```
p_d_ff_rst : process (clk, rst)
begin

    if rising_edge(clk) then
        if (rst = '1') then
            q      <= '0';
            q_bar <= '1';
        else
            q      <= d;
            q_bar <= not d;
        end if;
    end if;
end process p_d_ff_rst;
```

Listing of VHDL clock, reset and stimulus processes from the testbench file for both D type flip-flops:

```
p_clk_gen : process
begin
    while now < 1000 ns loop
        s_clk <= '0';
        wait for c_CLK_PERIOD / 2;
        s_clk <= '1';
        wait for c_CLK_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

p_reset_gen : process
begin
    s_arst <= '0';
    wait for 58 ns;
    s_arst <= '1';
    wait for 10 ns;
```

```

    assert(s_q = '0' and s_q_bar = '1')
    report "reset error" severity error;
    wait for 5 ns;
    s_arst <= '0';
    wait for 30 ns;
    s_arst <= '1';
    wait;
end process p_reset_gen;


p_stimulus : process
begin
    report "Stimulus process started" severity note;
    s_d <= '0';
    wait for 13ns;
    s_d <= '1';
    wait for 10ns;
    s_d <= '0';
    wait for 5ns;
    assert(s_q = '0' and s_q_bar = '1')
    report "ff error" severity error;
    wait for 5 ns;
    s_d <= '1';
    wait for 5ns;
    assert(s_q = '1' and s_q_bar = '0')
    report "ff error" severity error;
    wait for 5 ns;
    s_d <= '0';
    wait for 10ns;
    s_d <= '1';
    wait for 10ns;
    s_d <= '1';
    wait for 10ns;
    s_d <= '0';
    wait for 10ns;
    s_d <= '1';
    wait for 10ns;
    s_d <= '0';

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;


```

*"arst" changes to "rst" and vice versa

 Screenshot with simulated time waveforms for D type flip-flop with an async reset:



 Screenshot with simulated time waveforms for D type flip-flop with a sync reset:



VHDL code listing for JK type flip-flop with a sync reset:

```
architecture Behavioral of jk_ff_rst is
    signal s_q : std_logic;
begin

    p_jk_ff_rst : process (clk)
    begin
        if rising_edge(clk) then
            if (rst = '1') then
                s_q <= '0';
            else
                if (j = '0' and k = '0') then
                    s_q <= s_q;
                elsif (j = '1' and k = '0') then
                    s_q <= '1';
                elsif (j = '0' and k = '1') then
                    s_q <= '0';
                elsif (j = '1' and k = '1') then
                    s_q <= not s_q;
                end if;
            end if;
        end if;
    end process p_jk_ff_rst;

    q <= s_q;
    q_bar <= not s_q;

end Behavioral;
```

Listing of VHDL clock, reset and stimulus processes from the testbench file for JK type flip-flop:

```
p_clk_gen : process
begin
    while now < 1000 ns loop
        s_clk <= '0';
        wait for c_CLK_PERIOD / 2;
        s_clk <= '1';
        wait for c_CLK_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;
```

```


p_reset_gen : process
begin
    s_rst <= '0';
    wait for 43 ns;
    s_rst <= '1';
    wait for 10ns;
    assert(s_q = '0' and s_q_bar = '1')
    report "reset error" severity error;
    wait for 3 ns;
    s_rst <= '0';
    wait for 70 ns;
    s_rst <= '1';
    wait;
end process p_reset_gen;

p_stimulus : process
begin
    report "Stimulus process started" severity note;
    s_j <= '0';
    s_k <= '0';
    wait for 24ns;
    s_j <= '1';
    s_k <= '0';
    wait for 5ns;
    assert(s_q = '1' and s_q_bar = '0')
    report "ff error" severity error;
    wait for 35ns;
    s_j <= '0';
    s_k <= '1';
    wait for 5ns;
    assert(s_q = '0' and s_q_bar = '1')
    report "ff error" severity error;
    wait for 35ns;
    s_j <= '1';
    s_k <= '1';
    wait for 30ns;
    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;

```

*"arst" changes to "rst" and vice versa

 Screenshot with simulated time waveforms for JK type flip-flop with a sync reset:



VHDL code listing of the processes for T type flip-flop with a sync reset:

```

architecture Behavioral of t_ff_rst is
    signal s_q : std_logic;
begin
    p_d_ff_rst : process (clk, rst)
    begin
        if rising_edge(clk) then
            if (rst = '1') then
                s_q <= '0';
            elsif (t = '1') then
                s_q <= not s_q;
            else
                s_q <= s_q;
            end if;
        end if;
    end process p_d_ff_rst;
    q <= s_q;
    q_bar <= s_q;
end Behavioral;

```

Listing of VHDL clock, reset and stimulus processes from the testbench file for T type flip-flop:

```

p_clk_gen : process
begin
    while now < 1000 ns loop
        s_clk <= '0';
        wait for c_CLK_PERIOD / 2;
        s_clk <= '1';
        wait for c_CLK_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

p_reset_gen : process
begin
    s_rst <= '0';
    wait for 10 ns;
    s_rst <= '1';
    wait for 13 ns;
    s_rst <= '0';
    wait for 80 ns;
    s_rst <= '1';
    wait for 10 ns;
    assert(s_q = '0' and s_q_bar = '1')
    report "reset error" severity error;
    wait for 20 ns;
    s_rst <= '0';
    wait;
end process p_reset_gen;

p_stimulus : process
begin

```




```

report "Stimulus process started" severity note;
s_t <= '0';
wait for 13ns;
s_t <= '1';
wait for 30ns;
s_t <= '0';
wait for 50ns;
s_t <= '1';
wait for 50ns;
s_t <= '0';
wait for 50ns;
s_t <= '1';
wait for 50ns;
s_t <= '1';
wait for 50ns;
s_t <= '0';

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

 Screenshot with simulated time waveforms for T type flip-flop with a sync reset:



4. Shift register

Image of the shift register schematic:
shift_register_4bit

