

0 - Traffic lights

1. Preparation tasks

State table:

| | | | | | | | | | | | | | | | | |
|----------|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| Input P | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| Clock | ↑ | ↑ | ↑ | ↑ | ↑ | ↑ | ↑ | ↑ | ↑ | ↑ | ↑ | ↑ | ↑ | ↑ | ↑ | ↑ |
| State | A | A | B | C | C | D | A | B | C | D | B | B | B | C | D | B |
| Output R | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 |

Figure with connection of RGB LEDs on Nexys A7 board:


 


Table with color settings:

| RGB LED | Artix-7 pin names | Red | Yellow | Green |
|---------|-------------------|-------|--------|-------|
| LD16 | N15, M16, R12 | 1,0,0 | 1,1,0 | 0,1,0 |
| LD17 | N16, R11, G14 | 1,0,0 | 1,1,0 | 0,1,0 |

2. Traffic light controller

State diagram:

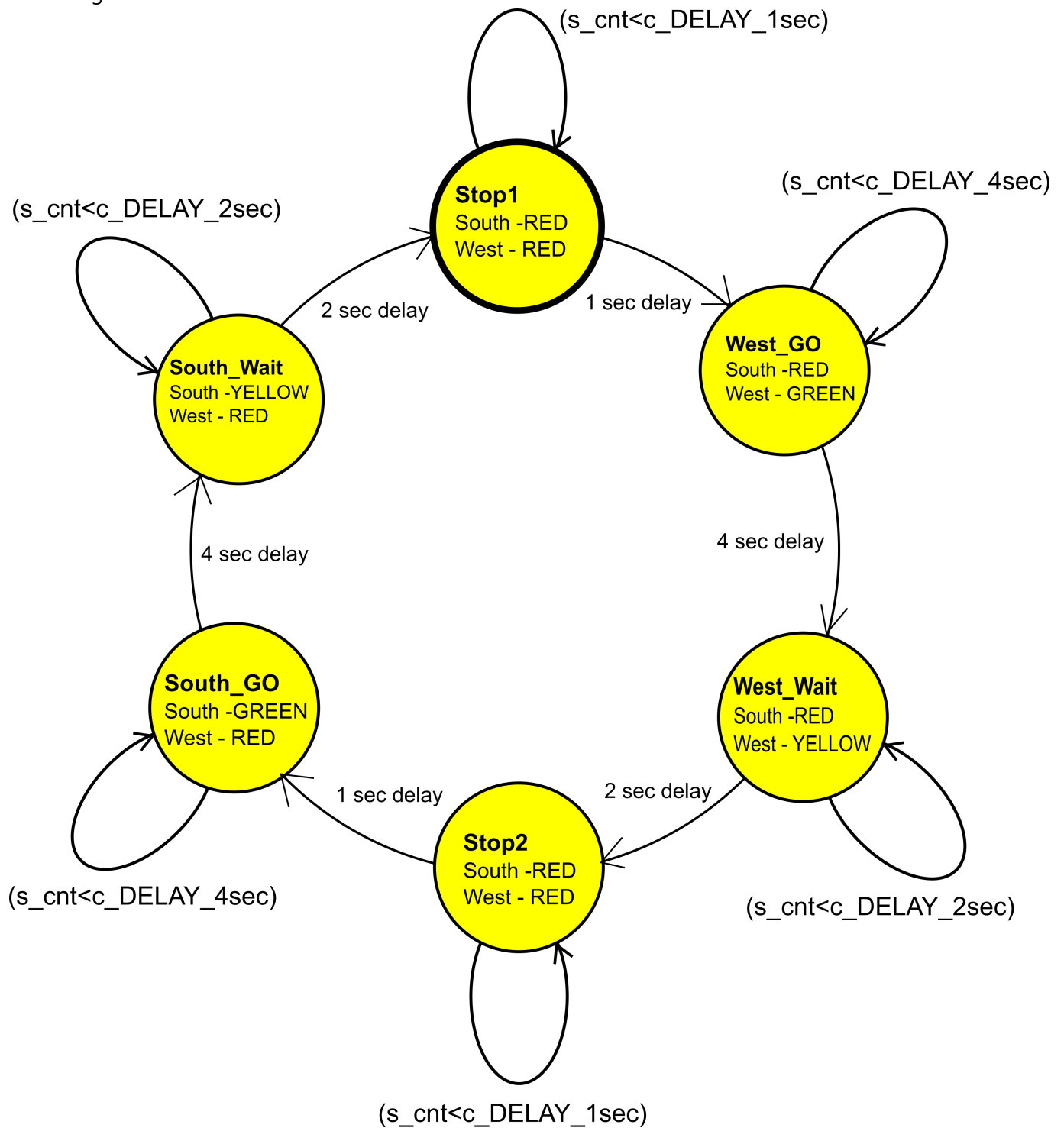

Listing of VHDL code of sequential process `p_traffic_fsm`:

```

p_traffic_fsm : process(clk)
begin
    if rising_edge(clk) then
        if (reset = '1') then
            s_state <= STOP1 ;
            s_cnt <= c_ZERO;
            -- Synchronous reset
            -- Set initial state
            -- Clear all bits

        elsif (s_en = '1') then
            -- Every 250 ms, CASE checks the value of the s_state
            -- variable and changes to the next state according

```

```
-- to the delay value.
case s_state is

    -- If the current state is STOP1, then wait 1 sec
    -- and move to the next GO_WAIT state.
    when STOP1 =>
        -- Count up to c_DELAY_1SEC
        if (s_cnt < c_DELAY_1SEC) then
            s_cnt <= s_cnt + 1;
        else
            -- Move to the next state
            s_state <= WEST_GO;
            -- Reset local counter value
            s_cnt <= c_ZERO;
        end if;

    when WEST_GO =>
        if (s_cnt < c_DELAY_4SEC) then
            s_cnt <= s_cnt + 1;
        else
            s_state <= WEST_WAIT;
            s_cnt <= c_ZERO;
        end if;
    when WEST_WAIT =>
        if (s_cnt < c_DELAY_2SEC) then
            s_cnt <= s_cnt + 1;
        else
            s_state <= STOP2;
            s_cnt <= c_ZERO;
        end if;
    when STOP2 =>
        if (s_cnt < c_DELAY_1SEC) then
            s_cnt <= s_cnt + 1;
        else
            s_state <= SOUTH_GO;
            s_cnt <= c_ZERO;
        end if;
    when SOUTH_GO =>
        if (s_cnt < c_DELAY_4SEC) then
            s_cnt <= s_cnt + 1;
        else
            s_state <= SOUTH_WAIT;
            s_cnt <= c_ZERO;
        end if;
    when SOUTH_WAIT =>
        if (s_cnt < c_DELAY_2SEC) then
            s_cnt <= s_cnt + 1;
        else
            s_state <= STOP1;
            s_cnt <= c_ZERO;
        end if;

    -- It is a good programming practice to use the
    -- OTHERS clause, even if all CASE choices have
    -- been made.
```

```

        when others =>
            s_state <= STOP1;

        end case;
    end if; -- Synchronous reset
end if; -- Rising edge
end process p_traffic_fsm;

```

Listing of VHDL code of combinatorial process `p_output_fsm`


```

p_output_fsm : process(s_state)
begin
    case s_state is
        when STOP1 =>
            south_o <= c_RED;
            west_o  <= c_RED;
        when WEST_GO =>
            south_o <= c_RED;
            west_o  <= c_GREEN;
        when WEST_WAIT =>
            south_o <= c_RED;
            west_o  <= c_YELLOW;
        when STOP2 =>
            south_o <= c_RED;
            west_o  <= c_RED;
        when SOUTH_GO =>
            south_o <= c_GREEN;
            west_o  <= c_RED;
        when SOUTH_WAIT =>
            south_o <= c_YELLOW;
            west_o  <= c_RED;
        when others =>
            south_o <= c_RED;
            west_o  <= c_RED;
    end case;
end process p_output_fsm;


```

Screenshots of the simulation:

Reset:

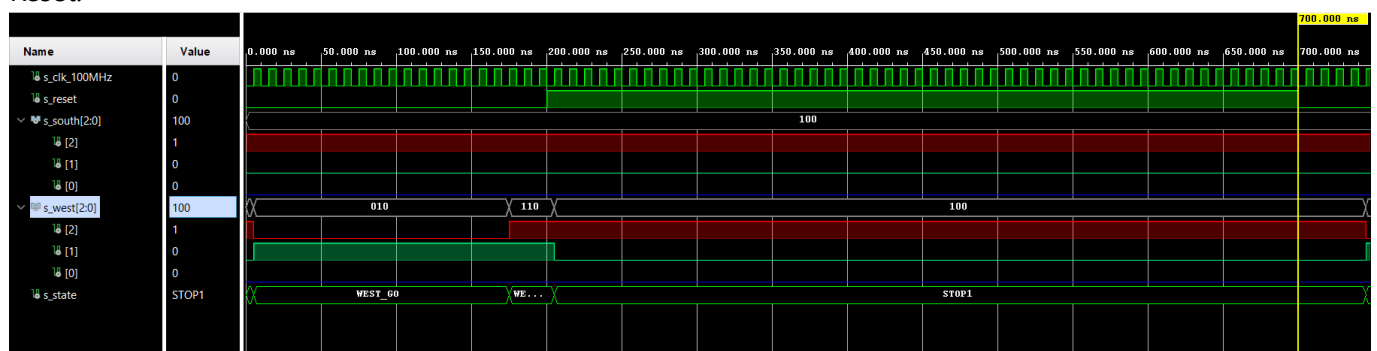

Cycle:

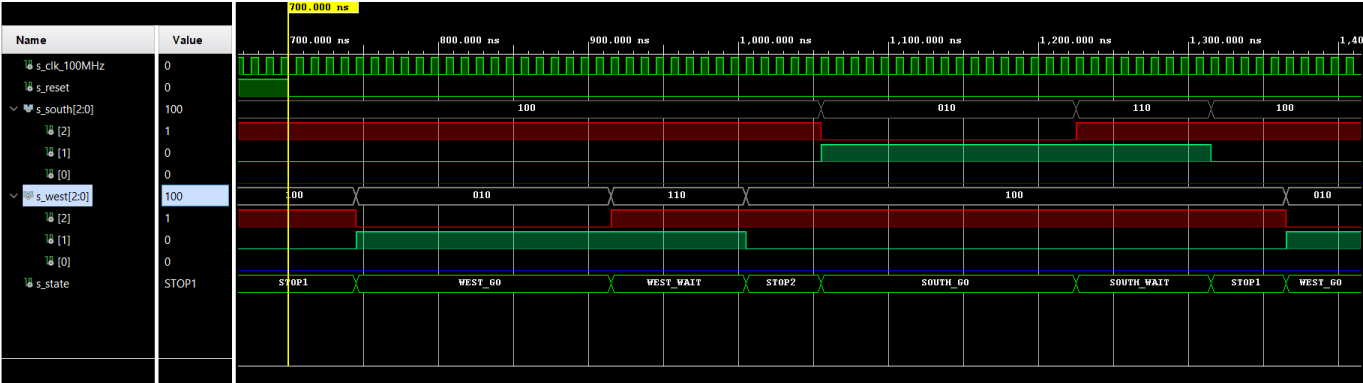


3. Smart controller

State table:

| Current state | Direction South | Direction West | Sensor South | Sensor West | Next state |
|---------------|-----------------|----------------|--------------|-------------|------------|
| STOP1 | red | red | X | X | WEST_GO |
| WEST_GO | red | green | 0 | 0 | WEST_GO |
| WEST_GO | red | green | 0 | 1 | WEST_GO |
| WEST_GO | red | green | 1 | 0 | WEST_WAIT |
| WEST_GO | red | green | 1 | 1 | WEST_WAIT |
| WEST_WAIT | red | yellow | X | X | STOP2 |
| STOP2 | red | red | X | X | SOUTH_GO |
| SOUTH_GO | green | red | 0 | 0 | SOUTH_GO |
| SOUTH_GO | green | red | 0 | 1 | SOUTH_WAIT |
| SOUTH_GO | green | red | 1 | 0 | SOUTH_GO |
| SOUTH_GO | green | red | 1 | 1 | SOUTH_WAIT |
| SOUTH_WAIT | yellow | red | X | X | STOP1 |

State diagram:

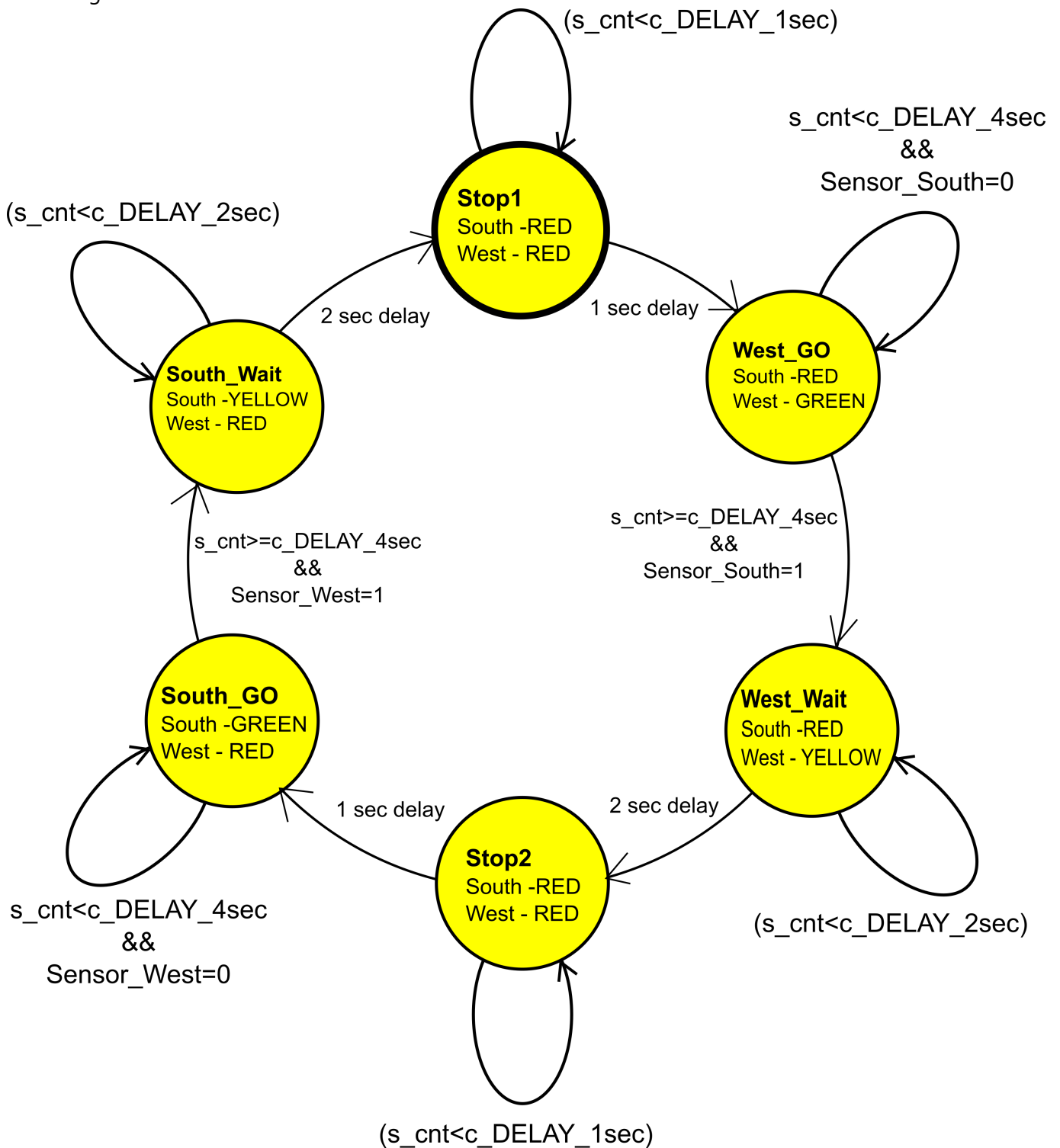

Listing of VHDL code of sequential process `p_smart_traffic_fsm`:

```

p_smart_traffic_fsm : process(clk)
begin
    if rising_edge(clk) then
        if (reset = '1') then
            s_state <= STOP1 ;
            s_cnt <= c_ZERO;
            -- Synchronous reset
            -- Set initial state
            -- Clear all bits

        elsif (s_en = '1') then
            case s_state is

```

```

when STOP1 =>
    if (s_cnt < c_DELAY_1SEC) then
        s_cnt <= s_cnt + 1;
    else
        s_state <= WEST_GO;
        s_cnt <= c_ZERO;
    end if;
when WEST_GO =>
    if (s_cnt < c_DELAY_4SEC) then
        s_cnt <= s_cnt + 1;
    elsif (sensor_south_i='0') then
        s_cnt <= c_DELAY_4SEC; -- trochu bodge, ale aspon
ochrani proti preteceniu s_cnt
    else
        s_state <= WEST_WAIT;
        s_cnt <= c_ZERO;
    end if;
when WEST_WAIT =>
    if (s_cnt < c_DELAY_2SEC) then
        s_cnt <= s_cnt + 1;
    else
        s_state <= STOP2;
        s_cnt <= c_ZERO;
    end if;
when STOP2 =>
    if (s_cnt < c_DELAY_1SEC) then
        s_cnt <= s_cnt + 1;
    else
        s_state <= SOUTH_GO;
        s_cnt <= c_ZERO;
    end if;
when SOUTH_GO =>
    if (s_cnt < c_DELAY_4SEC) then
        s_cnt <= s_cnt + 1;
    elsif (sensor_west_i='0') then
        s_cnt <= c_DELAY_4SEC;
    else
        s_state <= SOUTH_WAIT;
        s_cnt <= c_ZERO;
    end if;
when SOUTH_WAIT =>
    if (s_cnt < c_DELAY_2SEC) then
        s_cnt <= s_cnt + 1;
    else
        s_state <= STOP1;
        s_cnt <= c_ZERO;
    end if;
when others =>
    s_state <= STOP1;

end case;
end if; -- Synchronous reset
end if; -- Rising edge
end process p_smart_traffic_fsm;

```

