

# 04 - Segment


---

## 1. Tables

Table with connection of 7-segment displays:

Pin No. at 0V	func.
U13	Disp. 7 ENABLED
K2	Disp. 6 ENABLED
T14	Disp. 5 ENABLED
P14	Disp. 4 ENABLED
J14	Disp. 3 ENABLED
T9	Disp. 2 ENABLED
J18	Disp. 1 ENABLED
J17	Disp. 0 ENABLED
T10	CA ON
R10	CB ON
K16	CC ON
K13	CD ON
P15	CE ON
T11	CF ON
L18	CG ON
H16	DP ON

Schematic:

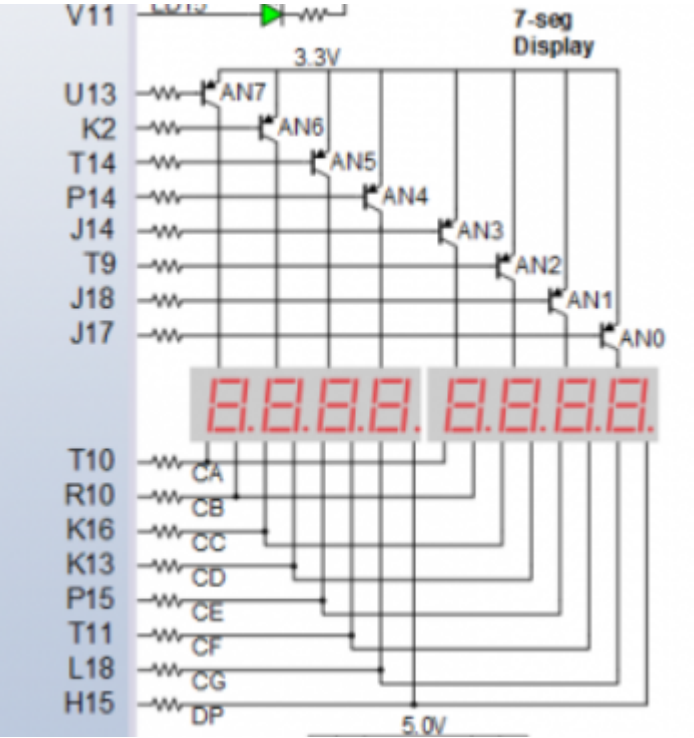

Decoder truth table for common anode 7-segment display:

Hex	Inputs	A	B	C	D	E	F	G
0	0000	0	0	0	0	0	0	1
1	0001	1	0	0	1	1	1	1
2	0010	0	0	1	0	0	1	0
3	0011	0	0	0	0	1	1	0
4	0100	1	0	0	1	1	0	0
5	0101	0	1	0	0	1	0	0
6	0110	0	1	0	0	0	0	0
7	0111	0	0	0	1	1	1	1
8	1000	0	0	0	0	0	0	0
9	1001	0	0	0	0	1	0	0
A	1010	0	0	0	1	0	0	0
b	1011	1	1	0	0	0	0	0
C	1100	0	1	1	0	0	0	1
d	1101	1	0	0	0	0	1	0
E	1110	0	1	1	0	0	0	0
F	1111	0	1	1	1	0	0	0

## 2. Seven-segment display decoder

VHDL architecture from source file hex\_7seg.vhd:

```
p_7seg_decoder : process(hex_i)
begin
    case hex_i is
        when "0000" =>
            seg_o <= "0000001";    -- 0
        when "0001" =>
            seg_o <= "1001111";    -- 1
        when "0010" =>
            seg_o <= "0010010";    -- 2
        when "0011" =>
            seg_o <= "0000110";    -- 3
        when "0100" =>
            seg_o <= "1001100";    -- 4
        when "0101" =>
            seg_o <= "0100100";    -- 5
        when "0110" =>
            seg_o <= "0100000";    -- 6
        when "0111" =>
            seg_o <= "0001111";    -- 7
        when "1000" =>
            seg_o <= "0000000";    -- 8
        when "1001" =>
            seg_o <= "0000100";    -- 9
        when "1010" =>
            seg_o <= "0001000";    -- A
        when "1011" =>
            seg_o <= "1100000";    -- b
        when "1100" =>
            seg_o <= "0110001";    -- C
        when "1101" =>
            seg_o <= "1000010";    -- d
        when "1110" =>
            seg_o <= "0110000";    -- E
        when others =>
            seg_o <= "0111000";    -- F
    end case;
end process p_7seg_decoder;
```

VHDL stimulus process from testbench file tb\_hex\_7seg.vhd:


```
p_stimulus : process
begin
    -- Report a note at the begining of stimulus process
    report "Stimulus process started" severity note;

    s_hex <= "0000"; wait for 50 ns;
```

```
s_hex <= "0001"; wait for 50 ns;
s_hex <= "0010"; wait for 50 ns;
s_hex <= "0011"; wait for 50 ns;
s_hex <= "0100"; wait for 50 ns;
s_hex <= "0101"; wait for 50 ns;
s_hex <= "0110"; wait for 50 ns;
s_hex <= "0111"; wait for 50 ns;
s_hex <= "1000"; wait for 50 ns;
s_hex <= "1001"; wait for 50 ns;
s_hex <= "1010"; wait for 50 ns;
s_hex <= "1011"; wait for 50 ns;
s_hex <= "1100"; wait for 50 ns;
s_hex <= "1101"; wait for 50 ns;
s_hex <= "1110"; wait for 50 ns;
s_hex <= "1111"; wait for 50 ns;

-- Report a note at the end of stimulus process
report "Stimulus process finished" severity note;
wait;
end process p_stimulus;
```

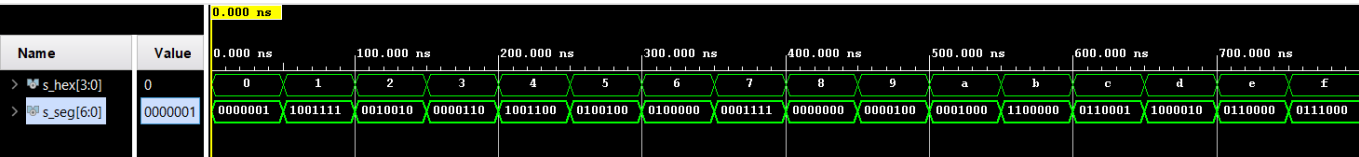Screenshot with simulated time waveforms:



VHDL code from source file top.vhd with 7-segment module instantiation:

```
hex2seg : entity work.hex_7seg
port map(
    hex_i    => SW,
    seg_o(6) => CA,
    seg_o(5) => CB,
    seg_o(4) => CC,
    seg_o(3) => CD,
    seg_o(2) => CE,
    seg_o(1) => CF,
    seg_o(0) => CG
);
```

3. LED(7:4) indicators

Truth table for LEDs(7:4):

Hex	Inputs	LED4	LED5	LED6	LED7
0	0000	1	0	0	0
1	0001	0	0	1	1

Hex	Inputs	LED4	LED5	LED6	LED7
2	0010	0	0	0	1
3	0011	0	0	1	0
4	0100	0	0	0	1
5	0101	0	0	1	0
6	0110	0	0	0	0
7	0111	0	0	1	0
8	1000	0	0	0	1
9	1001	0	0	1	0
A	1010	0	1	0	0
b	1011	0	1	1	0
C	1100	0	1	0	0
d	1101	0	1	1	0
E	1110	0	1	0	0
F	1111	0	1	1	0

VHDL code for LEDs(7:4):

```
-- Display input value on LEDs
LED(3 downto 0) <= SW;

-- LED(7:4) indicators
-- Turn LED(4) on if input value is equal to 0, ie "0000"
LED4 : process (SW)
begin
    if (SW = "0000") then
        LED(4) <= '1';
    else
        LED(4) <= '0';
    end if;
end process LED4;

-- Turn LED(5) on if input value is greater than "1001", ie 9
LED5 : process (SW)
begin
    if (SW > b"1001") then
        LED(5) <= '1';
    else
        LED(5) <= '0';
    end if;
end process LED5;
```

```
-- Turn LED(6) on if input value is odd, ie 1, 3, 5, ...
LED6 : process (SW)
begin
    if (SW(0) = '1') then
        LED(6) <= '1';
    else
        LED(6) <= '0';
    end if;
end process LED6;

-- Turn LED(7) on if input value is a power of two, ie 1, 2, 4, or 8
LED7 : process (SW)
begin
    case SW is
        when "0001" =>
            LED(7) <= '1';
        when "0010" =>
            LED(7) <= '1';
        when "0100" =>
            LED(7) <= '1';
        when "1000" =>
            LED(7) <= '1';
        when others =>
            LED(7) <= '0';
    end case;
end process LED7;
```

Screenshot with simulated time waveforms:

